MARK SCHEMES - Physics Unit 2 Homework

1) (a) earth	1
(b) it can prevent an electric shock from the toaster	1
(c) 230 V	1
(d) (the potential difference) for the alternating supply changes direction allow current	1
(the potential difference) for the alternating supply changes magnitude allow current allow converse allow potential difference of alternating supply is	
greater	1
2. (a) 17.8 accept 17.7 or 17.9	1
(b) potential difference = current \times resistance accept $V = IR$	1
(c) $3.22 = 2.18 \times R$	1
R = 3.22/2.18	1
R = 1.477(064) Ω	1
R = 1.48 (Ω) an answer of 1.48 (Ω) scores 4 marks an answer that rounds to 1.48 (Ω) scores 3 marks	1
(d) temperature of wire will increase during experiment allow description of this in terms of energy being dissipated, $P = I^2 R$	1
if constantan is used, this will not have a significant effect on results	1
renewable resources are replenished allow the converse	

(at least) as fast as they are used up

1

(b) (step-up) transformer between power station and grid increases p.d.

ս. 1

giving lower current


or

more efficient transmission

1

(step-down) transformer between grid and domestic users decreases pd

4) a)

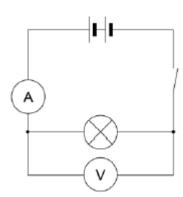

battery connected correct way round

1

ammeter and voltmeter correct way round

1

(b) (the lamp will) get dimmer

1

because increasing the resistance decreases the current

1

(c) 20 minutes = 1200 seconds

1

10 000 = I x 1200

1

I = 10000 / 1200

1

= 8.3

1

allow 8.3 with no working shown for 4 marks

Amps (A)

1